

BANGLADESH UNIVERSITY OF ENGINEERING AND TECHNOLOGY

Course No : CSE306

Course Name : Computer Architecture Sessional

Name of the Experiment : 4-bit ALU Simulation

Level/Term : 3-1

Section : B2

Group No : 02

Student ID : 1705092

1705111

1705116

1705118

1705121

Date of Submission : 28-03-2021

Introduction

An Arithmetic Logic unit or commonly known as ALU is a combinational digital circuit that performs arithmetic and logic operations on binary numbers. It is a simple binary calculator. It is a fundamental building block of many types of computing circuits, including the central processing unit (CPU) of computers. In this experiment, we have to design a 4-bit ALU according to design specification.


Problem Specification:

CS_2	CS_1	C_{in} CS_0	Function
0	0	0	Decrement A ($A-1$)
0	0	1	Transfer A (A)
0	1	0	Subtract with borrow ($A-B-1 = A+B'$)
0	1	1	Subtract ($A-B = A+B'+1$)
1	0	x	AND ($A \wedge B$)
1	1	x	Complement A (A')


Arithmetic Part

When $CS_2 = 0$ Arithmetic part will be activated.


- i. Decrement A (A-1) :

 


- ii. Transfer A (A) :

 

 - iii. Subtract with borrow ($A-B-1 = A+B'$) :



iv. Subtract ($A-B = A+B'+1$) :

 

Logic Part

When $CS_2 = 1$ Logic part will be activated. And if we look at our previous available arithmetic circuits, forcing $C_{in} = 0$ from the full adder output we get, $sum = x \oplus y$

For logic operation $A \wedge B$,

Let us assume $(A_i \vee K_i)$ in X_i and B'_i in Y_i .

$$\begin{aligned} Function &= (A + K) \oplus B' \\ &= (A + K).B + (A + K)'.B' \\ &= AB + KB + A'K'B' \end{aligned}$$

$$\text{Now, } AB = AB + KB + A'K'B'$$

$$\Rightarrow KB + A'K'B' = 0$$

$$\Rightarrow KB = 0$$

$$\therefore K = B'$$

$$\text{and, } A'K'B' = 0$$

$$\Rightarrow K'B' = 0$$

$$\therefore K = B'$$

Now if we construct our Function Table,

Function Table :

CS_2	CS_1	C_{in} CS_0	X_i	Y_i	Function
0	0	0	A_i	1	$A-1$
0	0	1	A_i	1	A
0	1	0	A_i	B'_i	$A+B'$
0	1	1	A_i	B'_i	$A+B'+1$
1	0	x	$A_i \vee B'_i$	B'_i	$A \wedge B$
1	1	x	A_i	1	A'

X_i :

K-Map:

$A_i B_i$					
		$CS_2 \ CS_1$	00	01	11
$CS_2 \ CS_1$	00	0	0	1	1
	01	0	0	1	1
	11	0	0	1	1
	10	1	0	1	1

$$X_i = A + CS_2 \cdot CS'_1 \cdot B'$$

Y_i :

Truth table:

CS_2	CS_1	Y_i
0	0	1
0	1	B_i'
1	0	B_i'
1	1	1

K-Map:

$CS_2 \backslash CS_1$		B_i	
		0	1
00	1	1	1
01	1	1	0
11	1	1	1
10	1	1	0

$$Y_i = B_i' + CS_2' \cdot CS_1' + CS_2 \cdot CS_1$$

$$\therefore Y_i = B_i' + (CS_2 \oplus CS_1)'$$

C_{in} :

When $CS_2 = 1$, CS_0 is don't care (x). We force 0 in C_{in} for logic operation. So,

K-Map:

CS_0/C_{out} $CS_2 \ CS_1$		CS_0/C_{out}	
		0	1
00	0	0	1
01	0	0	1
11	0	0	0
10	0	0	0

$$C_{in_1} = CS'_2 \cdot CS_0 \quad ; \text{ for the first full adder.}$$

$$C_{in_i} = CS'_2 \cdot C_{out_{i-1}} \quad ; \text{ for the rest three full adders.}$$

Flags

As we use forced C_{in} for our logic / bitwise operation, the C_{out} for flag output calculation is also considered as, $C_{out} \cdot CS'_2$. The Flags are designed accordingly to that.

$$CF = C_{out_4}$$

$$SF = F_4$$

$$ZF = (F_1 + F_2 + F_3 + F_4)'$$

$$VF = C_{out_4} \oplus C_{out_3}$$

Block Diagram

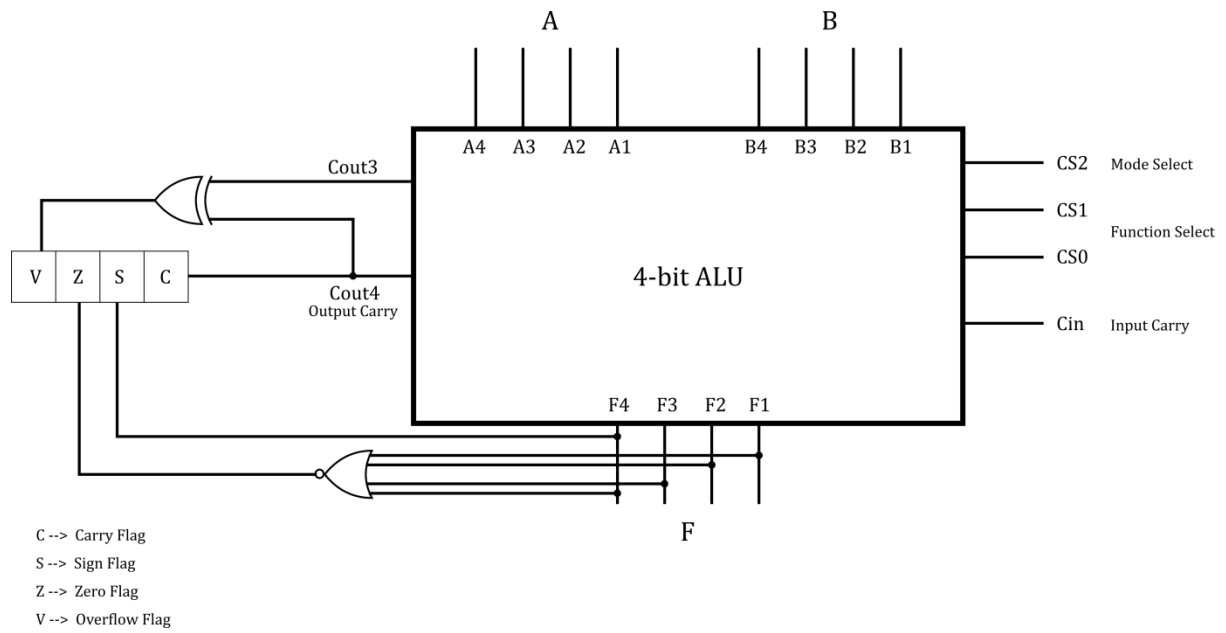


Figure : Block diagram of a 4-bit ALU

Complete Circuit Diagram

 


Figure : Circuit diagram of the 4-bit ALU

ICs used with count

Components	Count of Gates	IC Number	Count of ICs
NOT	6	IC74LS04	1
AND	13	IC74LS08	4
OR	10	IC74LS32	3
NOR	1	IC74LS02	1
XOR	1	IC74LS86	1
XNOR	4	IC4077	1
Adder	-	IC7483	4

Simulator used

The simulation software used in this 4-bit ALU simulation experiment is ***logisim-win-2.7.1.exe***

Discussion

In this experiment, we used the simulation software *logisim* to simulate a 4-bit Arithmetic Logic Unit.

As per specification when the mode selection bit CS_2 is 1 the ALU operates as logic unit and the selection bit CS_0 (C_{in}) is don't care. In our circuit design we forced C_{in} to be 0 to work in the logic operations.

And for the Flags to show accordingly, the carry out of each adder is considered to be the AND of CS'_2 and C_{out} .

We calculated the input signals of the adders to simplify the equations and minimize the IC count.